

Answer Sheet: Online Examination

Roll No.:	16010121045	
Course	EEEE	Page No
Date	25/2/22	1

Name of the student: Rangat Singh Dhanjal	Signature of the student: <u>Rangat</u>
--	--

Q1) A)

I) b) $V_{AB} = +18V, 3.6 \Omega$

II) d) 8V peak to peak and out of phase with input signal.

III) c) both P and N are lightly doped

IV) c) 30

V) a) DC cumulative compound motor

VI) c) $f_0/2$

VII) b) 6

VIII) d) a short circuit

IX) b) 90° X) d) 30°

Answer Sheet: Online Examination

Roll No.:	16010121045	
Course	EEEE	Page No
Date	25/2/22	2

Name of the student:

Pangat Singh Dhanjal

Signature of the student:

Pangat


Q1) B)

iv) The advantages of zener diode are:-

- zener diode is cheaper than other diodes
- Controls the flowing current.
- Can be used to regulate & stabilise voltage.
- Compatibility and obtainability.

v) Superposition theorem states that in a network of linear element containing more than one source of energy the voltage or current flowing across any load is the sum of all voltages or current which would result if each source is considered separately & all other sources are replaced with their internal resistances.

I)

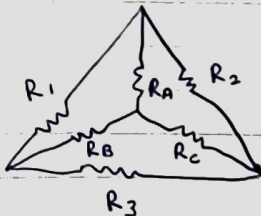

$$R_A = 8 \Omega, R_B = 11 \Omega, R_C = 15 \Omega$$

For star to delta transformation

$$R_1 = \frac{R_A R_B + R_B R_C + R_A R_C}{R_C} = \frac{8(11) + 11(15) + 15(8)}{15}$$


$$R_1 = 24.87 \Omega$$

$$R_2 = \frac{R_A R_B + R_B R_C + R_A R_C}{R_B} = \frac{8(11) + 11(15) + 15(8)}{11}$$


$$R_2 = 33.91 \Omega$$

$$R_3 = \frac{R_A R_B + R_B R_C + R_A R_C}{R_A} = \frac{8(11) + 11(15) + 15(8)}{8}$$

$$R_3 = 46.63 \Omega$$

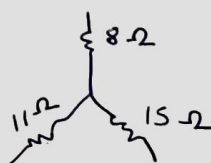

≡

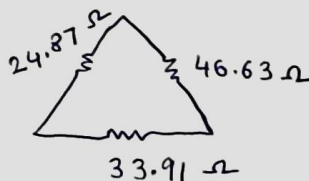

Answer Sheet: Online Examination

Roll No.:	16010121045	
Course	EEEE	Page No
Date	23/2/22	3

Name of the student:


Pangat Singh Dhanjal

Signature of the student:

Pangat.

Q1)B)

vii)

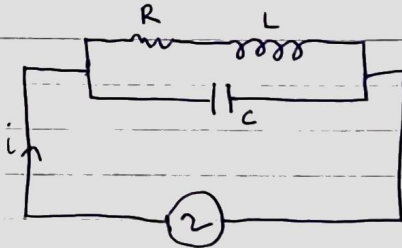where, $R = 9 \Omega$ $L = 0.12 \text{ H}$ $C = 330 \mu\text{F}$

To find Quality factor.

we know for // resonance circuit
 quality factor = $\frac{\omega R L}{R}$ \rightarrow ①

we also know $\omega R = \frac{1}{\sqrt{LC}}$

$$\therefore \omega R = \frac{1}{\sqrt{0.12 \times 330 \times 10^{-6}}} = \frac{10^3}{\sqrt{39.6}} = 0.1589 \times 10^3$$

inserting in equ ①

$$\theta = \frac{10^3 \times 0.1589 \times 0.12}{9} = 2.12$$

$$\therefore \theta = 2.12$$

Answer Sheet: Online Examination

Roll No.:	16010121045	
Course	EEEE	Page No
Date	23/2/22	4

Name of the student: Pangat Singh Dhanjal	Signature of the student: <u>Pangat</u>
--	--

~~Q1) A)~~

Q1) B)

II) $I_1 = 20 \sin(\omega t + \frac{\pi}{4})$ $I_2 = 14 \sin(\omega t - \frac{\pi}{6})$

$I_{1rms} = \frac{20}{\sqrt{2}} = 14.14 \text{ A}$ $I_{2rms} = 9.90 \text{ A}$


$\bar{I}_1 = 14.14 \angle 45^\circ = 9.998 + j9.998$

$\bar{I}_2 = 9.9 \angle -30^\circ = 8.57 - j4.95$

$\bar{I} = \bar{I}_1 + \bar{I}_2$
 $= 9.998 + 8.57 + j(9.998 - 4.95)$
 $= 18.568 + j5.048$

$\therefore \bar{I} = 19.24 \angle 15.20$

Q2) I)

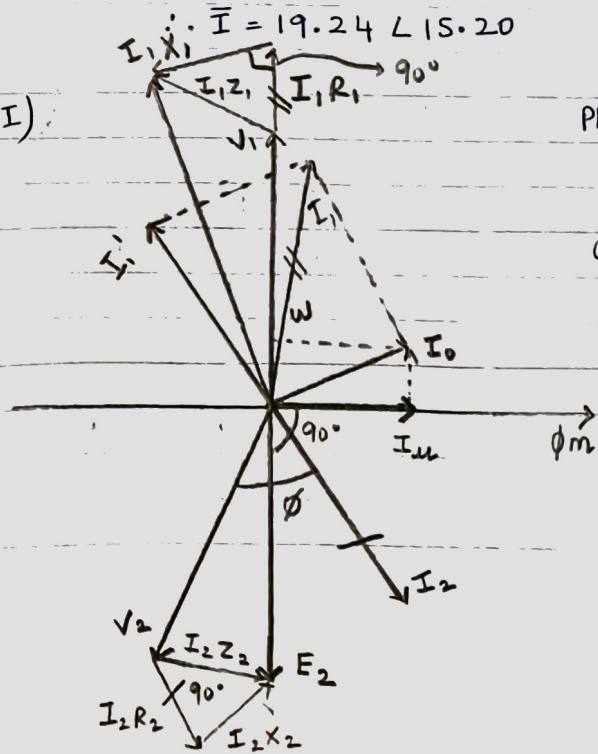


Phasor diagram of single phase transformer.

Capacitive load.

Answer Sheet: Online Examination

Roll No.:	16010121045	
Course	EEEE	Page No
Date	23/2/22	5

Name of the student: Pangat Singh Charyal	Signature of the student: <i>Pangat</i>
--	--

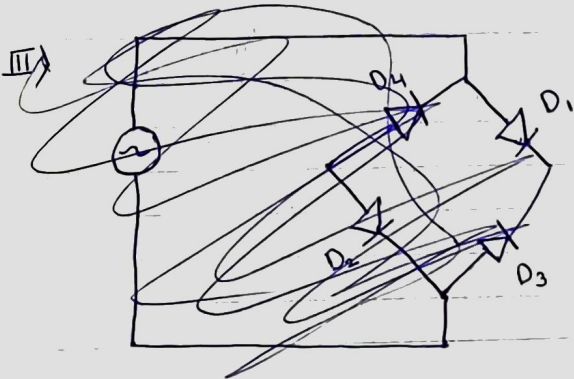

III)

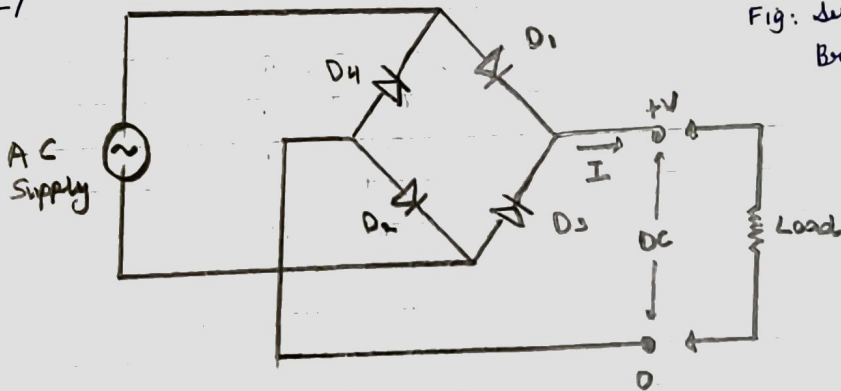



Fig: Single Phase Bridge rectifier.

working

- The circuit consists of two power diodes connected to a single load resistance (R_L) with each diode taking it, in turn to supply current to the load resistor.
- During positive half cycles, D_1 & D_2 are forward biased & D_3 & D_4 are reverse biased. When the voltage is greater than the threshold level of diodes D_1 & D_2 starts conducting.
- During negative half cycles, D_3 & D_4 are forward biased & D_1 & D_2 are reverse biased.
- In both cases the direction of load current is same. Hence we obtain a unidirectional current i.e. DC current. So we converted AC current \rightarrow DC current.

⑥

Q3)

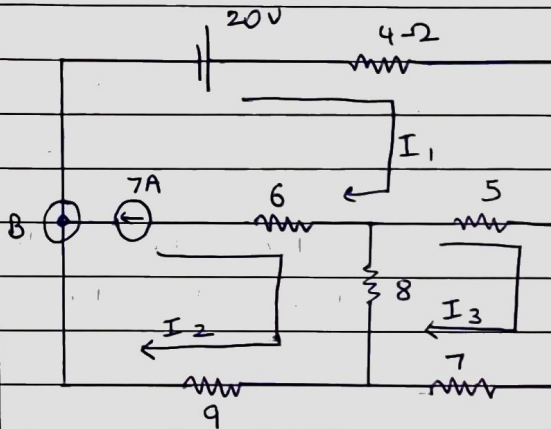

current source 7A on
common branch, hence
supermesh

$$\text{KCL at node B } I_2 + 7 = I_1$$

$$I_2 - I_1 = -7 \rightarrow \textcircled{1}$$

KVL ~~to~~ supermesh

$$20 - 4I_1 - 5(I_1 - I_3) - 8(I_2 - I_3) - 9I_2 = 0$$

$$20 - 4I_1 - 5I_1 + 5I_3 - 8I_2 + 8I_3 - 9I_2 = 0$$

$$20 + 13I_3 - 9I_1 - 17I_2 = 0$$

$$9I_1 + 17I_2 - 13I_3 = 20 \rightarrow \textcircled{2}$$

KVL at mesh 3

$$-5(I_3 - I_1) - 7I_3 - 8(I_3 - I_2) = 0$$

$$-5I_3 + 5I_1 - 7I_3 - 8I_3 + 8I_2 = 0$$

$$5I_1 + 8I_2 - 20I_3 = 0 \rightarrow \textcircled{3}$$


on solving $\textcircled{1}$ $\textcircled{2}$ $\textcircled{3}$

$$I_1 = 5.84 \text{ A} \quad I_2 = -1.15 \text{ A} \quad I_3 = 1 \text{ A}$$

$$\text{Power in } 9\Omega \text{ resistor} = I^2 R = (-1.15)^2 \times 9$$

$$\text{Power} = 11.9025 \text{ W}$$

Q4)

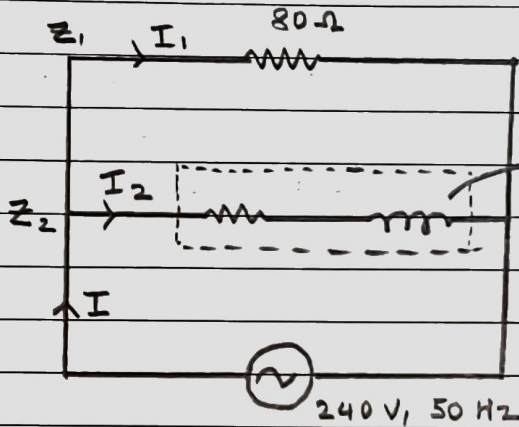

$$Z_1 = 80 \Omega$$

$$Z_2 = R + jXL$$

(consider R to be self-resistance)

∴ L be the inductance

We know, $I = \frac{V}{Z}$

$$I = 7A, V = 240V$$

$$\therefore Z = \frac{V}{I} = \frac{240 \angle 0}{7} = 34.29 \angle 0$$

$$Y_1 = \frac{1}{Z_1} = \frac{1}{80}$$

$$Y_2 = \frac{1}{Z_2} = \frac{1}{R + jXL}$$

$$\therefore Y = Y_1 + Y_2 = \frac{1}{80} + \frac{1}{R + jXL}$$

$$Y = \frac{(R + 80) + jXL}{80(R + jXL)}$$

$$\therefore Z = \frac{1}{Y} = \frac{80(R + jXL)}{(R + 80) + jXL} = 34.29 \angle 0$$

$$\therefore \frac{R + j 2\pi \cdot 50 \cdot L}{(R + 80) + j 2\pi 50 L} = 34.29 \angle 0 = 0.43 \angle 0$$